

$$V_Z = 6V, I_Z = 6mA, r_z = 25\Omega \text{ \& } I_{ZK} = 0.2mA$$

(a) No Load,  $V_o = ?$

$$\begin{aligned} \text{Sol}^n: V_{Z_0} &= 6 - 25 \times 6 \times 10^{-3} \\ &= 6 - 150 \times 10^{-3} \\ &= 6 - 0.15 \\ &= 5.85V \end{aligned}$$

$$I = \frac{15 - 5.85}{1025} = 8.926mA$$

$$\therefore V_o = 5.85 + \frac{8.926 \times 25}{1000} = 6.073V$$

$$\therefore \boxed{V_o = 6.073V}$$

(b)  $R_L = 4k\Omega$ ,  $\Delta V_o = ?$

$$\text{Sol}^n: i_L = \frac{6.073}{4000} = 0.001518 = 1.518mA$$

$$\therefore \Delta V_o = -25 \times \frac{1.518}{1000} = -0.03795V$$

$$\therefore \boxed{\Delta V_o = -37.950mV}$$


(c) Minimum value of  $R_L$  for which Zener diode will operate = ?

$$\text{Sol}^n: i_R = \frac{15 - 5.85}{1000} = 9.15mA$$

$$i_L = (9.15 - 0.2)mA = 8.95mA$$

$$\therefore R_{L_{min}} = \frac{5.85}{8.95} k\Omega = 0.65363 \times 1000\Omega$$
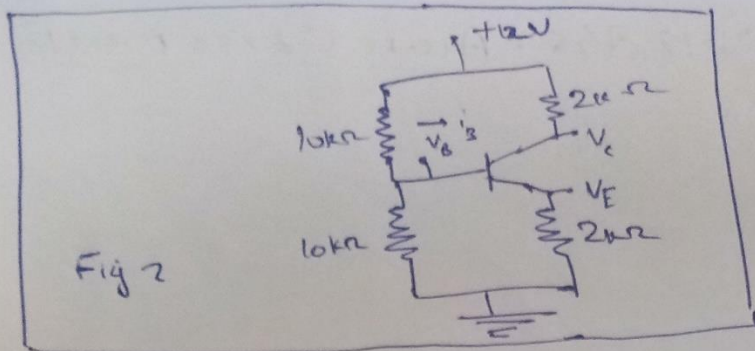
$$\therefore \boxed{R_{L_{min}} = 653.63\Omega}$$



$$i_B = \frac{12 - V_B}{10k} + \frac{0 - V_B}{10k}$$

$$\therefore V_B = 6 - (5k)i_B \quad \text{--- (i)}$$

$$\text{Now, } V_E = (2k) \cdot i_E$$

$$\text{Also, } V_{BE} = 0.6 \text{ V}$$

$$\therefore 6 - 5i_B - 2i_E = 0.6 \text{ V}$$

$$\therefore (5k)i_B + (2k)i_E = 5.4 \quad \text{--- (ii)}$$

$$\text{And } i_E = i_C + i_B = \beta i_B + i_B = (\beta + 1)i_B$$

$$\therefore i_E = (49 + 1)i_B = 50i_B \quad \text{--- (iii)}$$

$$\therefore i_B (105k) = 5.4 \quad \text{--- [from (ii) & (iii)]}$$

$$\therefore \boxed{i_B = 51.4 \mu\text{A}}$$

$$\text{Now, } i_C = \beta i_B = 49 \times 51.4 \times 10^{-3} \text{ mA} = 2.519 \text{ mA}$$

$$\therefore \boxed{i_C = 2.519 \text{ mA}}$$

$$i_E = 50 \times 51.4 \times 10^{-3} \text{ mA} \quad \text{--- [from (i)]}$$

$$\therefore \boxed{i_E = 2.571 \text{ mA}}$$

$$\therefore V_B = 6 - 5 \times 51.4 \times 10^{-3} = 5.742 \text{ V}$$

$$\therefore \boxed{V_B = 5.742 \text{ V}} \quad \rightarrow \quad V_E = 5.142 - 0.6$$

$$\boxed{V_E = 5.142}$$


$$V_C = 12 - 2 \times 2.519 = 6.962 \text{ V}$$

$$\therefore \boxed{V_C = 6.962 \text{ V}}$$

Since,  $V_{BE} < 0$   
&  $V_{BE} > 0$   
 $\therefore$  The Mode  
of operation  
is **FORWARD  
ACTIVE**



3.  
Soln

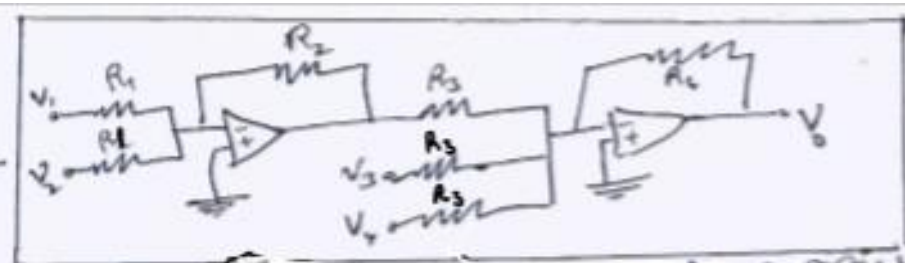

Let's derive a general expression for  $V_0$

$$V_0 = V_1 \left( -\frac{R_2}{R_1} \right) \left( -\frac{R_4}{R_3} \right) + V_2 \left( -\frac{R_2}{R_1} \right) \left( -\frac{R_4}{R_3} \right) - \frac{R_4}{R_3} V_3 - \frac{R_4}{R_3} V_4$$

$$= (V_1 + V_2) \left( \frac{R_2 R_4}{R_1 R_3} \right) - \left( \frac{R_4}{R_3} \right) (V_3 + V_4)$$

$$\boxed{V_0 = (V_1 + V_2) \left( \frac{R_2 R_4}{R_1 R_3} \right) - (V_3 + V_4) \left( \frac{R_4}{R_3} \right)} \quad \text{--- ①}$$

(a) If all the Resistors are  $= R$ .

$$\boxed{V_0 = V_1 + V_2 - V_3 - V_4} \quad \dots \text{[from ①]}$$

(b)  $R_1 = R$ ,  $R_2 = 2R$ ,  $R_3 = 4R$ ,  $R_4 = 6R$

From ①,


$$\therefore V_0 = (V_1 + V_2) \frac{(2R)(6R)}{(R)(4R)} - \left( \frac{6R}{4R} \right) (V_3 + V_4)$$

$$= 3(V_1 + V_2) - \frac{3}{2} (V_3 + V_4)$$

$$= 3 \left[ V_1 + V_2 - \frac{V_3}{2} - \frac{V_4}{2} \right]$$

$$\boxed{V_0 = 3 \left( V_1 + V_2 - \frac{V_3}{2} - \frac{V_4}{2} \right)}$$

4.  
Sol<sup>n</sup>

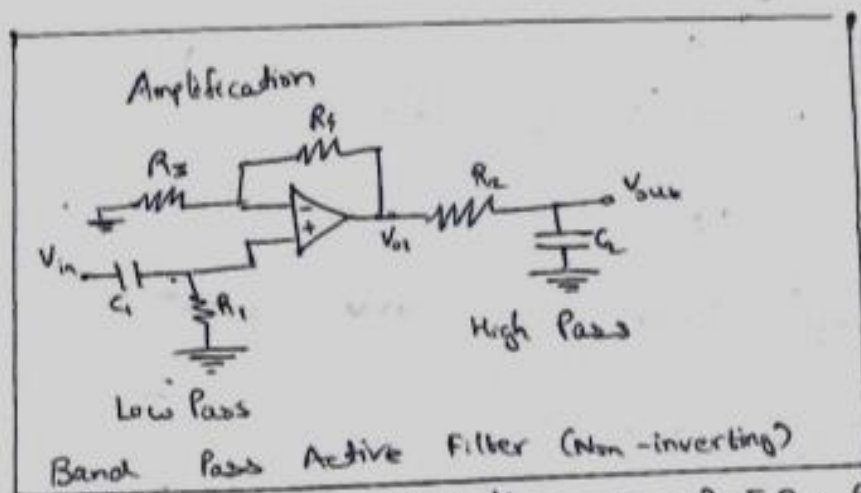

$$C_1 = C_L$$

$$C_2 = C_H$$

$$f_L = 1500 \text{ Hz}, f_H = 3700 \text{ Hz}, R_1 = R_2 = R_3 = R_4 = 2.3 \text{ k}\Omega$$

$$\text{Band Pass Gain (BPG)} = \left(1 + \frac{R_4}{R_3}\right) = (1 + 1) = 2 \quad \therefore \text{BPG} = 2$$

$$(i) C_L = \frac{1}{2\pi R f_L} = \frac{1}{2\pi \times 2.3 \times 15 \times 10^5} = 0.00461 \times 10^{-5} \text{ F}$$

$$\therefore C_L = 46.1 \text{ nF} \quad \dots \text{ (Low Pass Capacitance)}$$

$$C_H = \frac{1}{2\pi R f_H} = \frac{1}{2\pi \times 2.3 \times 37 \times 10^5} = 0.00187 \times 10^{-5} \text{ F}$$

$$\therefore C_H = 18.7 \text{ nF} \quad \dots \text{ (High Pass Capacitance)}$$

$$(ii) \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + \left(\frac{f}{3700}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{f}{1500}\right)^2}} \times 2 \times \frac{f}{f_L}$$

$$= \frac{1}{750} \times \frac{f}{\sqrt{\left(1 + \left(\frac{f}{3700}\right)^2\right) \left(1 + \left(\frac{f}{1500}\right)^2\right)}}$$

$$\therefore V_{out} = \frac{V_{in} f}{750 \sqrt{\left(1 + \left(\frac{f}{3700}\right)^2\right) \left(1 + \left(\frac{f}{1500}\right)^2\right)}}$$

4. (iii)

(a)  $f = f_L/4 = 1500/4 = 375 \text{ Hz}$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{2} \cdot \frac{1}{375} \times \frac{375}{\sqrt{1 + \left(\frac{375}{3700}\right)^2} \sqrt{1 + \left(\frac{1}{4}\right)^2}}$$

$$= \frac{1}{2} \cdot \frac{4}{\sqrt{1.01027} \sqrt{17}} = 0.4824$$

$$\therefore V_{out} = (0.4824) V_{in}$$

(b)  $f = f_L$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{375} \times \frac{1500}{\sqrt{1 + \left(\frac{1500}{3700}\right)^2} \sqrt{1 + 1}} \times \frac{1}{2}$$

$$= \frac{1}{2} \cdot \frac{2\sqrt{2}}{\sqrt{1.16435}} = 1.3106$$

$$\therefore V_{out} = (1.3106) V_{in}$$

(c)  $f = f_H$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{2} \cdot \frac{1}{375} \times \frac{(3700)}{\sqrt{1 + 1^2} \sqrt{1 + \left(\frac{3700}{1500}\right)^2}}$$

$$= \frac{1}{2} \cdot \frac{9.867}{\sqrt{2} \sqrt{7.0844}} = 1.3106$$

$$\therefore V_{out} = (1.3106) V_{in}$$

(d)  $f = 4f_H$


$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{2} \cdot \frac{1}{375} \times \frac{4 \times 3700}{\sqrt{1 + 4^2} \sqrt{1 + \left(\frac{4 \times 3700}{1500}\right)^2}}$$

$$= \frac{39.468}{\sqrt{17} \sqrt{98351}} \cdot \frac{1}{2} = 0.4824$$

$$\therefore V_{out} = (0.4824) V_{in}$$



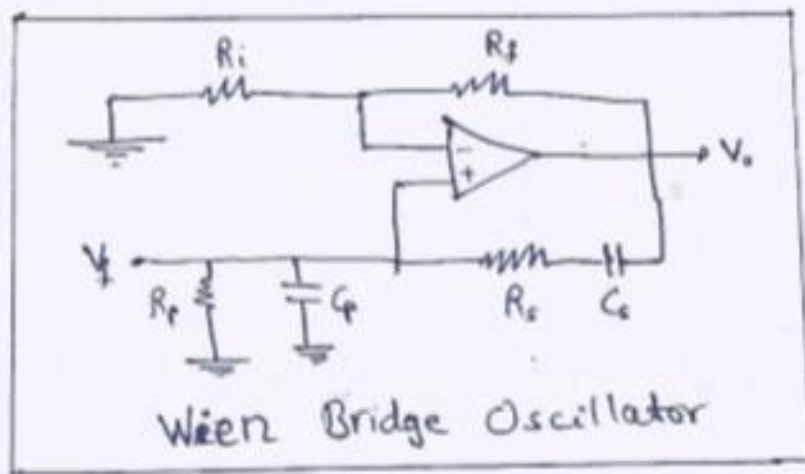5.  $R_s = 5 \text{ k}\Omega$ ,  $R_p = 12 \text{ k}\Omega$ ,  $C_s = 47 \text{ nF}$ ,  $C_p = 35 \text{ nF}$   
 Here based on the terminologies,  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 12 \text{ k}\Omega$ ,  $C_1 = 47 \text{ nF}$  &  $C_2 = 35 \text{ nF}$




(i) As we know,

$$\begin{aligned} \beta &= \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega (R_1 C_1 + R_2 C_2 + R_2 C_1)} \\ &= \frac{j\omega (12 \times 10^3) (47 \times 10^{-9})}{1 - \omega^2 (12 \times 5 \times 10^6) (47 \times 35 \times 10^{-18}) + j\omega (5 \times 47 + 35 \times 12 + 12 \times 47) \times 10^{-6}} \\ &= \frac{j\omega (564) \times 10^{-6}}{1 - \omega^2 (987 \times 10^{-10}) + j\omega (1219) \times 10^{-6}} \\ &= \frac{j\omega (564)}{10^6 - \omega^2 (987 \times 10^{-4}) + j\omega (1219)} \\ &= \frac{j\omega}{1773.049 - \omega^2 (1.75 \times 10^{-4}) + j\omega (2.161)} \end{aligned}$$

$$\therefore \beta = \frac{j\omega}{1773.049 - \omega^2 (1.75 \times 10^{-4}) + j\omega (2.161)}$$

$$\begin{aligned} \text{(ii)} \quad f &= \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{2\pi \sqrt{5 \times 10^3 \times 12 \times 47 \times 35 \times 10^{-18}}} = \frac{1}{2\pi \sqrt{987 \times 10^{-10}}} \\ &= \frac{10^5}{2\pi \sqrt{987}} = 506.595 \text{ Hz} \end{aligned}$$
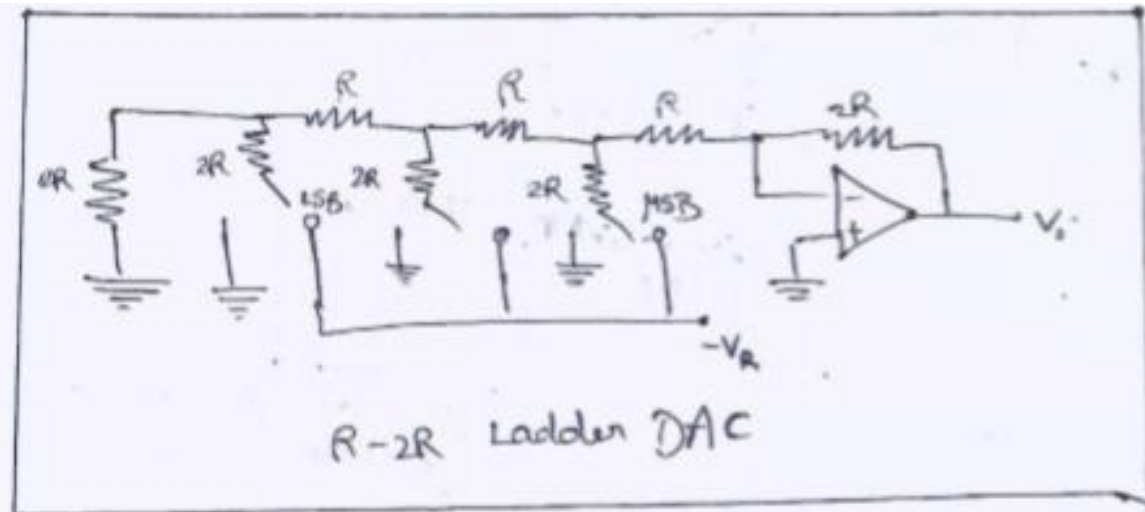
$$\therefore \boxed{f = 506.595 \text{ Hz}} \quad \text{for } \omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad \& \quad \beta \text{ to be real}$$



(i) For an N-bit ADC, having R-2R ladder,

$$V_o = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_{k=0}^{N-1} s_k 2^k$$

Here,  $n = 3$ ,  $R_f = 2R$ ,  $R_{Th} = 2R$  (As there even number of 2R resistors)  
 $V_R = -V_R$

$$\therefore V_o = -\frac{2R}{2R} \frac{(-V_R)}{2^3} (s_0 2^0 + s_1 2^1 + s_2 2^2)$$

$$= +\frac{V_R}{8} (s_0 2^0 + s_1 2^1 + s_2 2^2)$$

$$\therefore V_o = +\frac{V_R}{8} (s_0 + 2s_1 + 4s_2)$$

(ii) (a) Input sequence: 011  
 $s_2 s_1 s_0$

$$\therefore V_o = +\frac{V_R}{8} (1 + 2)$$


$$\therefore V_o = +\frac{3V_R}{8}$$

(b) Input Sequence: 101  
 $s_2 s_1 s_0$

$$\therefore V_o = +\frac{5V_R}{8}$$

(c) Input Sequence: 111

$$\therefore V_o = +\frac{7V_R}{8}$$

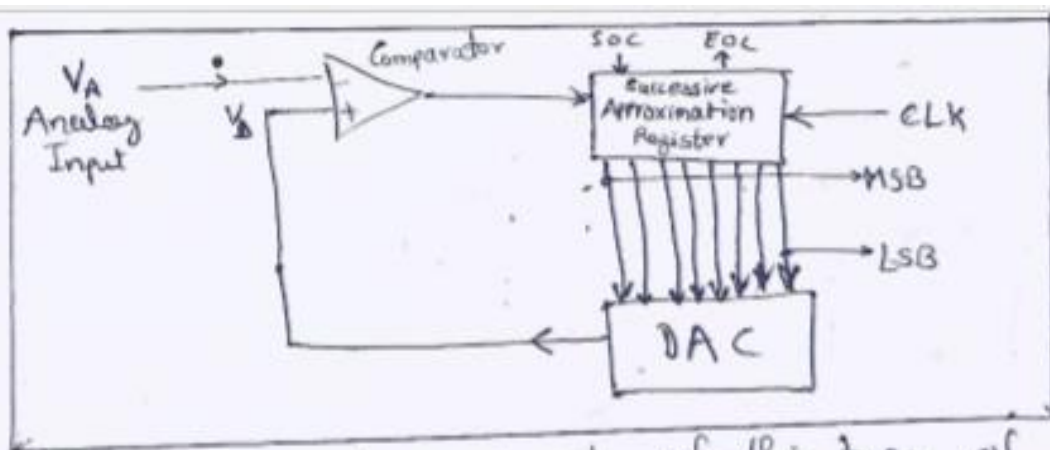

The basic principle of this type of A/D Converter is that - the unknown analog input voltage is approximated against an  $n$ -bit digital value by trying one bit at a time, beginning with the MSB.

This type of ADC operates by successively dividing the voltage range by half, as explained in the following steps:

- (1) The MSB is initially set to 1 with the remaining remaining 7 bits set as 0000000. The digital equivalent voltage is compared with the unknown analog input voltage.
- (2) If the analog input voltage is higher than the digital equivalent voltage, the MSB is retained as 1 and the second MSB is set to 1. Otherwise, the MSB is set to 0 and the second MSB is set to 1. Comparison is made as given in step (1) to decide whether to retain or reset the second MSB.

An 8-bit ADC was used. In order to find the input voltage we know the output signal = 01100101.  
Hence, the input voltage would have been =  $2^6 + 2^5 + 2^2 + 1$ .

$$V_A = 101V$$

From here we have to reverse Engineer how the conversion would have started.

- (i) MSB bit is set to 1  
 $V_D = [10000000]_2 = 128V > V_A = 101V$

- (ii)  $\therefore V_D = [01000000]_2 = 64V < V_A = 101V$

- (iii) Then, keep the next bit as 1  
 $V_D = [01100000]_2 = 96V < V_A = 101V$

Step taken	Status
(1)	Not Approved
(2)	Approved
(1)	Approved



7.

(iv) Again keep the next bit as 1

$$V_D = [01110000]_2 = 112V > V_A = 101V$$

(v)  $\therefore V_D = [01101000]_2 = 104V > V_A = 101V$

(vi)  $\therefore V_D = [01100100]_2 = 100V < V_A = 101V$

(vii) Now,  $V_D = [01100110]_2 = 102V > V_A = 101V$

(viii) Finally,  $V_D = [01100101]_2 = 101V = (V_A = 101V)$

Step	Status
(1)	Not Approved
(2)	Not Approved
(2)	Approved
(1)	Not Approve
(2)	Approved & Accepted

This is how we got the output digital sequence as 01100101.